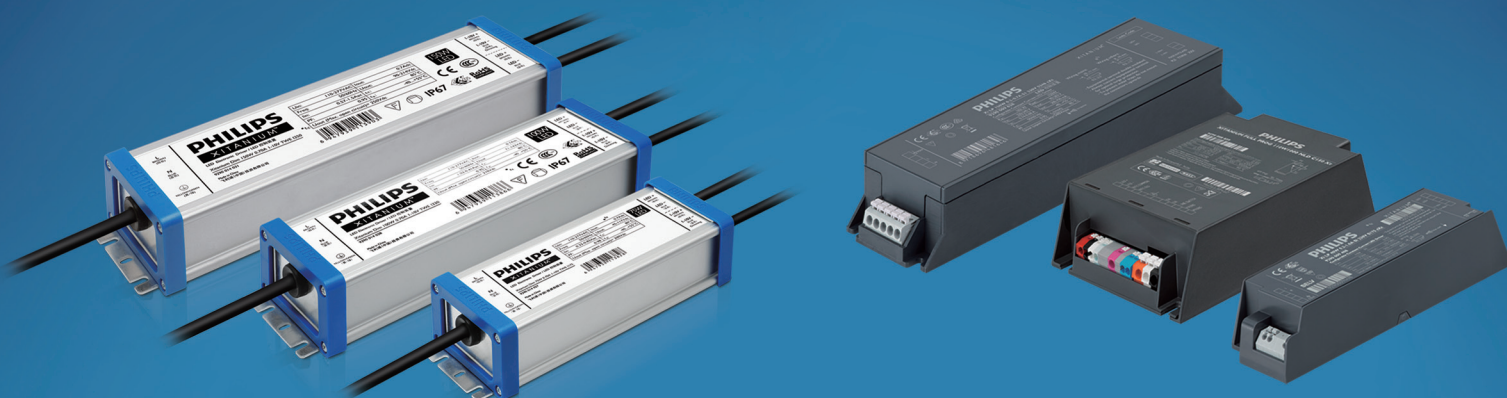


PHILIPS

Xitanium

LED outdoor drivers



Design-in Guide

Enabling **future-proof**
LED technology for
dynamic LED markets

December, 2021

Published versions

July, 2020

August, 2020

June, 2021

August, 2021

December, 2021

Contents


Contents	3
Introduction to this guide	5
Applications	5
Information or support	5
Determine which documents contain what information	5
Safety precautions	6
Safety warnings and instructions	6
Introduction to Xitanium Outdoor LED Drivers	7
Introduction	7
Xitanium LED driver versions	7
Features	7
Naming of the LED outdoor drivers	10
Electrical Design-in	11
Operating window	11
How to... Select an appropriate driver	12
Driver wiring and pinning	12
Adjustable Output Current (AOC) –set the driver output current	13
How to... Determine AOC priority with LED drivers	13
How to... Set the output current via Rset	15
How to... Set the output current via LEDset	15
How to... Program the output current	20
Mains voltage fluctuations	21
Inrush current	22
How to... Determine the number of drivers on a MCB	23
Surge protection	24
Leakage current	24
Electromagnetic compatibility (EMC)	25
How to... Improve EMI performance	26
Electrical isolation and protective earth	27

Thermal Design-In	30
Introduction	30
Definitions	30
Case Temperature Point (T _c point)	30
How to... Measure T _c at the T _c point	30
Relationship between T _c and ambient temperature	31
Driver lifetime	31
Module Temperature Protection (MTP)	31
Mechanical Design-In	33
IP rating	33
Installation	34
Controllability	37
Control characteristics	37
Non-dimmable	37
1-10V Dimming	38
DALI	39
PWM	39
Integrated programmable dimming protocols	40
How to... Connect to and program driver	44
How to... See the programming taking effect	44
Configurability	45
Introduction	45
Philips MultiOne Interface tool	45
Philips MultiOne Software	46
System requirements	46
Getting Started	46
MultiOne System	47
Settings	47
Quality and Reliability	48
Switching & cycling lifetime of LED drivers	48
Electrical failures due to switching V _{mains} on and off	48
Mechanical failures due to thermal cycling	48
Compliance and approval	51
Disclaimer	52

Introduction to this guide



IP67 Independent version

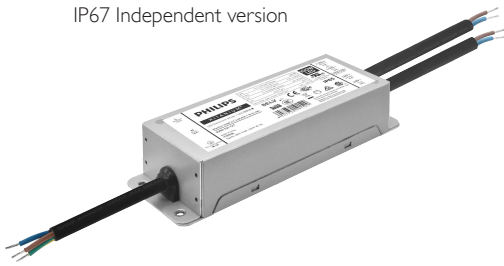


IP65 Independent version



Built-in version



Built-in version

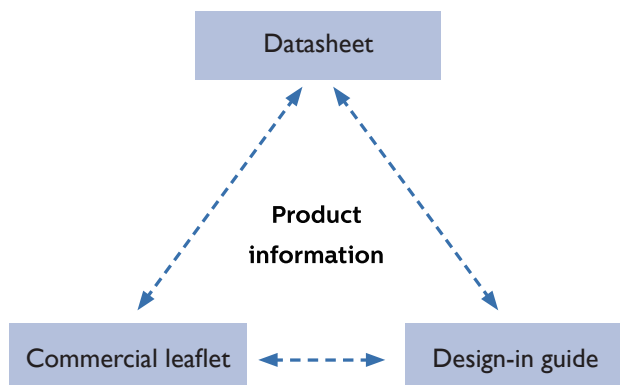

Thank you for choosing Philips Xitanium Outdoor LED drivers. In this guide you will find the information needed to integrate these drivers into a LED luminaire or LED system.

This edition describes the Xitanium Outdoor LED drivers optimized for outdoor application. We advise you to consult our websites for the latest up-to-date information.

Applications

The Xitanium Outdoor LED drivers are designed to operate LED solutions for outdoor lighting, like industrial, street, road lighting and open area environments. If you use Philips LED drivers in combination with Philips LED modules, specific design-in guides are available from below mentioned technology websites.

Classification

The Xitanium outdoor driver listed as below can be used in both Class I and Class II IEC isolation systems.

Information or support

Please consult your local Philips office or visit:
www.philips.com/technology

Determine which documents contain what information

In order to provide information in the best possible way, Philips' philosophy on product documentation is the following.

- **Commercial leaflet** contains product family information & system combinations
- **Datasheet** contains the product specific specifications
- **Design-in guide** describes how the product is to be designed-in

All these documents can be found on the download page of the OEM website www.philips.com/technology. If you require any further information or support please consult your local Philips office.

Safety precautions



Warnings:


- Avoid touching live parts!
- Do not use drivers with damaged housing and/or connectors!
- Do not use drivers with damaged wiring!
- Class I luminaires must be connected to protective earth!
- Do not service the driver when the mains voltage is connected; this includes connecting or disconnecting the LED load.
- Switchable function to make the open load on the driver output is abnormal condition, it is not an intended application that be allowed.
- For the driver claimed class II isolation, the EQUI must connected with luminaire grounding reference.

Safety warnings and instructions

- Do not use damaged or defective contacts or housings.
- Do not use damaged products.
- Cap off all unused wires to prevent accidental contact with the luminaire or driver housing.
- For the drivers with IP-rated connectors, the installers shall check that the seal of the connector is present and not damaged before connecting the male/female connectors.
- For connector version drivers, when luminaire manufacturers choose to cut off the connector, the original IP-rating cannot be guaranteed and becomes the responsibility of the luminaire manufacturers.
- The luminaire manufacturer is responsible for its own luminaire design and has to comply with all relevant safety standards.
- Philips offers the LED outdoor drivers with two different housing designs, built-in and independent. The built-in type drivers should not be exposed to the elements such as snow, water and ice. Exposure will lead to corrosion and even failure of the driver what should be avoided. It is the luminaire manufacturer's responsibility to prevent exposure. The independent type drivers can be exposed to the outdoor elements and installed apart from fixture.

Philips Design-in support is available; please contact your Philips sales representative.

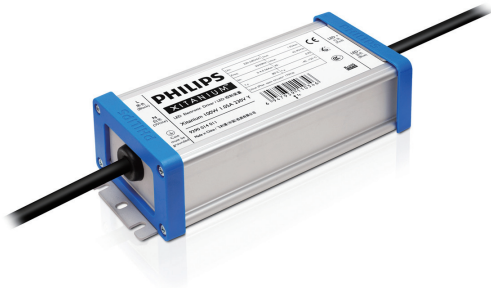
Introduction to Xitanium Outdoor LED Drivers



IP67 Independent version



Built-in version

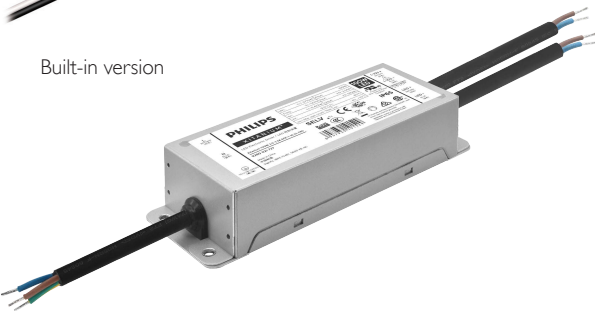

IP65 Independent version



IP65 round shape Highbay Independent version

Introduction

Xitanium Outdoor LED drivers are designed to operate LED solutions for outdoor lighting applications such as flood, street, road lighting as well as open area environments.

The operating points are chosen specifically to match the most commonly used LEDs.

Xitanium LED driver versions

The Xitanium LED drivers described in this guide are available in different versions, e.g. fixed-output and dimmable (1-10V; PWM; Line Switch; DALI), in a wide range of power ratings that enable the most popular light output levels for general lighting applications. We recommend you always check our Xitanium LED driver leaflet for the most up-to-date overview of our range. This leaflet can be found on the www.philips.com/technology website.

Features

Adjustable Output Current (AOC)

Flexibility in luminaire design is ensured by the adjustable output current (AOC).

The adjustable output current enables operation of various LED configurations from different LED manufacturers whilst also ensuring the solution remains “future proof” for new LED generations. The output current can be set with an external resistor (Rset). With our Programmable drivers, the output current setting can also be programmed using the Philips MultiOne programming hardware interface and the matching software “MultiOne driver configurator”.

More information about AOC and how to set the output current can be found in the chapter “Electrical design”



Controllability

The Xitanium Outdoor LED drivers are available in 3 different versions:

- Fixed Output
- 1-10V dimming
- DALI
- PWM
- Line Switch
- Amp Dim
- Communication (FELV) terminals marked “Risk of electric shock” are not safe to touch

Warning: Circuits connected to any FELV control terminal shall be insulated for the LV supply voltage of the controlgear and any terminals connected to the FELV circuit shall be protected against accidental contact.

The way of controlling is shown in the name of the driver. If no dimming protocol is given in the name, the Xitanium driver can only be used as a fixed output driver. The output current can be set as described in the Electrical design chapter. More information about the dimming protocols can be found in the Controllability chapter.

Thermal de-rating

Thermal de-rating of your LED PCB is possible by integrating an NTC (Negative Thermal Coefficient) component on the LED PCB and connect this NTC to the driver's NTC input. More details about the NTC resistor can be found in the Chapter “Temperature design”

Module Temperature Protection (MTP, adjustable on programmable drivers only)

This feature helps to protect the LEDs when operated in a hot ambient environment. The driver helps to regulate LED module temperature by regulating the output current. An NTC (Negative Temperature Coefficient resistor) must be present on the LED module and connected to respective pins on the driver in order to be able to make use this feature. Programmable drivers allow for changing the dimming behavior:

More information can be found under chapter Thermal Management.

Constant Light Output (CLO, programmable drivers only)

Traditional light sources suffer from depreciation in light output over time. This applies to LED light sources as well. The CLO feature enables LED solutions to deliver constant lumen output through the life of the light engine. Based on the type of LEDs used, heat management and driver current, it is possible to estimate the depreciation of light output for specific LEDs and this information can be entered into the driver. The driver counts the number of light source working hours and will increase output current based on this input to enable CLO. Since the CLO curve is not generic, the OEM needs to determine the appropriate CLO curve. This can be used to differentiate on e.g. lumen output or power consumption over lifetime.

The CLO feature can be programmed with the Philips MultiOne configurator tool. More information can be found on www.philips.com/multione

DC operation

It is possible to connect the mains side of the Xitanium driver to a DC power net (e.g. central emergency system). Check for input requirements the drivers' datasheet which can be found on www.philips.com/technology

For the DC operation, the external DC fuse must be used in the luminaire.

Naming of the LED outdoor drivers

Example:


1. Xitanium 150W 1.05A 230V I175C I67

Xitanium:	Brand name for reliable, affordable LED drivers
150W:	Maximum output power
1.05A:	Output current
230V:	Mains AC input voltage
I175 :	Housing length I (Independent housing design)
C :	Connector version
I67:	IP rating

2. Xi FP 150W 0.2-0.7A SNLDAE prog + 230V S240 sXt

Xi:	Xitanium(Xi)
Driver family:	SR (sensor ready) FP (full prog) LP (lite prog)
150W:	Maximum output power
0.2-0.7A:	Output current range
SNLDAE:	S (simpleset) N (NTC input) L (line switch) D (DALI) A (AmpDim) E (DC Emergency) M (Energy Meter) P (Auxiliary Power supply)
230V:	Mains AC input voltage
S240:	Housing length S (stretch) C (compact)

Electrical Design-in

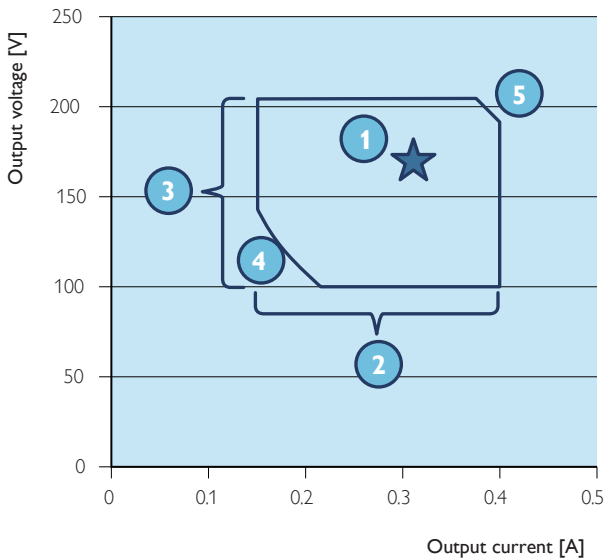

1. Required set point for the LED solution
2. Current can be set to needs within range
3. Driver adapts to required voltage, given it fits range
4. Driver minimum power limit
5. Driver maximum power limit

Example Operating window of a Xitanium driver

Note: by means of dimming it is possible to go below the minimum value of the specified output current.

Operating window

LED technology is rapidly evolving. Using more efficient LEDs in a next generation means the same light output can be achieved with lower currents. At the same time, LEDs can be driven at different currents levels based on the application requirement. Typically, LED drivers are available in discrete current levels e.g. 350mA, 500mA or 700mA. It is often necessary to replace a driver when more efficient LEDs or different LED boards become available.

One of the key features of the Xitanium LED drivers is the adjustable output current (AOC), offering flexibility and future-proof luminaire design. The Xitanium drivers can operate in a certain “operating window”. This window is defined by the maximum and minimum voltage and current that the driver can handle. An example of an operating window is shown on the left. The area indicates the possible current /voltage combinations. The current you select will depend on the type and manufacturer of the LEDs or the specific LED configuration of the PCB design. The voltage is the sum of the LEDs used (total Vf string). The operating window of every driver can be found in the datasheets which can be downloaded on following website:

www.philips.com/technology

1. Drivers with SimpleSet® functionality can be configured using the Philips MultiOne software and SimpleSet® interface.
2. DALI driver versions can be programmed both via SimpleSet and DALI interface. More information can be obtained at www.philips.com/multiOne.


Note: by means of testing the accuracy of the output current, the condition is required as below:

- Iout tolerance $\leq 5\%$ @ $T_a = 25^\circ\text{C}$ is tested @ 0 hour (cold start)
- Warning: Iout may have $\sim 20\text{mA}$ shift according to different T_c .

* Note: when connecting Philips LED Lines to the driver; the type of LED board (LV or HV) determines this requirement. Hybrid LED boards can be used on both type of drivers, indicated in commercial leaflet LED Lines, to be found in the download section of www.philips.com/technology

** Note: for Philips LED Lines standard system configurations, driven at nominal current, are stated in the commercial leaflet LED Lines, to be found in the download section of www.philips.com/technology

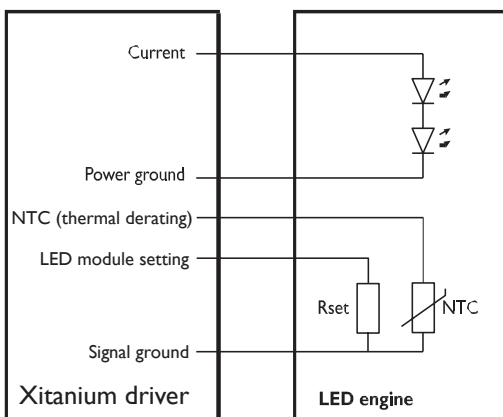Note: for a HV scenario that allows a 2 chain parallel solution, you are likely to find with steps described a lower rated driver power (e.g. 75 W for 1 chain versus 36 W for 2 chain solution)



Schematically representation of the drivers' output interfaces

How to... Select an appropriate driver

Depending on your requirements several drivers can be found as a solution for you. The following steps can help selecting the preferred driver:

For a full overview of available driver models, please refer to the commercial leaflet Xitanium Outdoor LED drivers, to be found in the download section of www.philips.com/technology, as are the datasheets associated with the drivers you intend to use.

1. Determine your required drive current (I_{drive}) and voltage (V_f)
2. Calculate required power via $P_{drive} = V_f \times I_{drive}$ (W)
3. Determine which type* of driver you need; Isolated or Non-isolated. Collect the associated datasheets from the website.
4. Does required current fit current range of driver?
- $I_{driver\ minimum} \leq I_{drive} \leq I_{driver\ maximum}$
5. Does required voltage fit voltage range of driver?
- $V_{driver\ minimum} \leq V_f \leq V_{driver\ maximum}$
6. Does required power fit power range of driver?
- $P_{driver\ minimum} \leq P_{drive} \leq P_{driver\ maximum}$
7. Choose your type** of dimming

Driver wiring and pinning

Driver lead wires with corresponding functions can be seen in figures on the left. The function of each wire will be discussed further in detail in the following chapters.

Note: currently all the Xitanium Outdoor LED drivers are single channel drivers. This means that for drivers with a double "+" and "-" output (see figure on the left) that these outputs are simply in parallel.

Adjustable Output Current (AOC) –set the driver output current

Output current can be set by placing an external resistor (LEDset and Rset) into the driver's Rset input. Next to that DALI driver versions allow also setting of the output current via software configuration.

Note: Rset is used as generic indication for Rset1, Rset2 or LEDset.

Note: LEDset and Rset-interface are not meant to be used as a control or dimming interface (for instance 1...10V). If this is not observed, both performance and safety requirements of the installation may be affected.

Programming enabled		
Yes	No	
	Rset connected	
	Yes	No
I_{nom} = Programmed value	I_{nom} = Rset Determined value	I_{nom} = $I_{default}$
Driver output current I_{nom} should always be $I_{driver\ min} \leq I_{nom} \leq I_{driver\ max}$		

Priority selection criteria for Group 1 - 1% minimum dim level

How to... Determine AOC priority with LED drivers

Since the DALI drivers allow two methods to set the output current (AOC), it is good to take note of the priority of each method with respect to the other:

Historically there are two groups of DALI drivers; those which can dim down to 1% (newer) and those which can dim down to 10% (older).

Group 1: 10% minimum dim level (newer drivers)

AOC programming has priority over Rset. For the priority selection criteria see table on the left.

Group 2: >1% minimum dim level (older drivers, 5% or 10% minimum dim level)

The value that sets the lowest current has priority over the other:

1. $I_{programming} < I_{Rset}$? => priority for $I_{programming}$
2. $I_{Rset} < I_{programming}$? => priority for I_{Rset}

E.g. programming 200 mA has priority over Rset which would generate 250 mA.

And Rset that generates 200 mA has priority over programming 250 mA.

Note: default current is stated in the driver's datasheet in the download section on www.philips.com/technology.



Example of a Set'n'drive resistor featured by BJB, fitted with a leaded resistor inside and allowing both manual or robot placement

How to... Set the output current via Rset

Your lumen, your current

1 resistor value generates 1 current only at all window drivers as long as it fits within the driver window.

That is 1 philosophy for all window drivers.

Why a resistor?

- Worldwide standardized building block
- Worldwide availability and well documented
- Freedom for OEM to choose the value and supplier

Resistor placed into driver enables you to

- Connect different configurations, not just a unique solution
- Drive different type of LED boards, not restricted to one type
- Select and tune the current, hence flux or Tc

Resistor characteristics



By making use of a resistor component with a determined Ohm value you can set the required current for your LED module. This component can be a leaded standard 1% tolerance resistor of e.g. 0.125 W or 0.25 W, 50 V. Rset will not be part of the electrical chain driving the LEDs, meaning it does not dissipate power. However, make sure it does not come into contact with the driver's housing. For safety reasons with non-isolated drivers the resistor must be insulated. Advice is to always insulate the resistor. Examples of a resistor placed into the drivers' input is shown on the left.


2 different Rset resistors are utilized in the Xitanium programmable LED driver portfolio;

- Rset1 (older drivers); allows output current setting up to 700 mA
- Rset2; allows output current setting up to 2000 mA


In all documentation, Rset may refer to either Rset1 or Rset2, depending on the driver type. Please check the driver datasheet for which Rset (1 and/or 2) the driver you use reads.

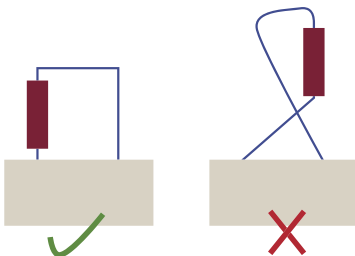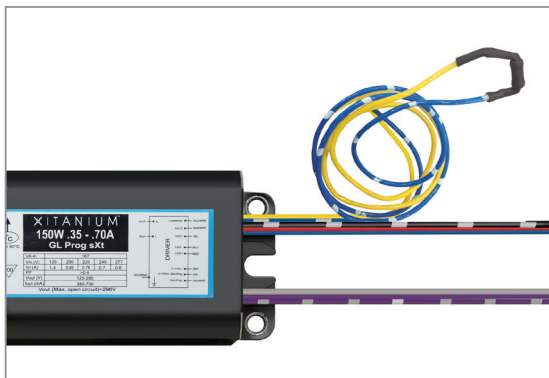Note: While inserting the resistor, please refer to the image on the left. The resistor must be inserted such that there is no possibility of a short caused by the leads. Especially when using non-isolated drivers, make sure the leads of the resistor are insulated. This way they cannot generate a potential safety risk, nor can the trip the earth leakage circuit breaker.



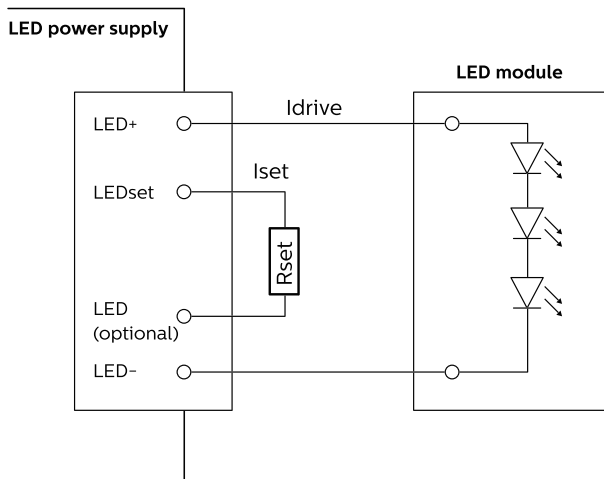

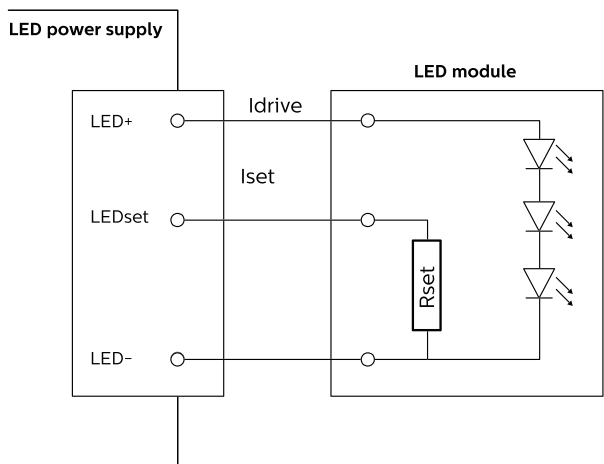Rset resistor mounted directly onto the driver



Rset resistor mounted onto the LED module

Rset1 and Rset2 use different pins on the driver

The Rset1 and Rset2 values with the corresponding drive currents are shown in following tables. It is advised to select the nearest lower resistor value that is available to you, if the exact determined value is not at hand.

How to... Set the output current via LEDset

Rset 1 and Rset 2 have been the traditional ways to set the current in the Xitanium window drivers. Next generation drivers will now be introduced with LEDset. LEDset is introduced by several vendors in the market to provide an industry standardized Rset interface. LEDset is, in essence, like Rset1 and Rset2, where one resistor value leads to one output current value only, differing only in the look-up table. Please find the table for E96 resistor values in the next section.

What does LEDset offer


Like Rset1 and Rset2, LEDset is an analogue interface, allowing basic current setting. The interface supports the following functions:

- Output current setting of the constant current LED driver to LED modules
- Thermal protection of the LED module(s) via thermal dynamic resistors circuit

How does LEDset work

LEDset is based on a 3 wire connection between LED driver and one or more LED modules as shown in the figure on the left. Only one additional wire, besides the two LED current supply wires, is used for transferring information from the LED module(s) to the LED driver; provided the Rset is mounted on the LED module.

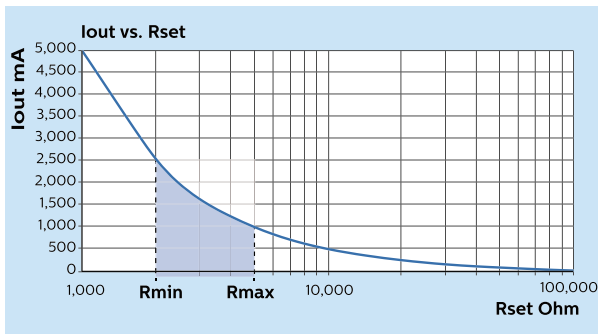Alternatively a standard resistor can be put directly into the driver's LEDset input connectors.



The LEDset interface measures the current I_{set} which flows from a 5V constant voltage source within the LED driver through the setting resistor(s) R_{set} which is/are located either on the LED modules or directly into the driver's R_{set} -input.

The current I_{set} flowing through one setting resistor R_{set} is determined by the equation:

$$I_{set} [A] = 5 [V] / R_{set} [\Omega]$$

A LED driver with LEDset interface is able to measure I_{set} and to set the LED driver output current I_{drive} dependent on the measured value of I_{set} according to the equation

$$I_{drive} = I_{set} \times 1000 [A]$$

Therefore the overall relationship between the setting resistor and the LED driver output current I_{drive} is then given by


$$I_{drive} [A] = (5 [V] / R_{set} [\Omega]) \times 1000$$

To calculate the required resistor value for a desired drive current I_{drive} use:

$$R_{set} [\Omega] = (5 [V] / I_{drive} [A]) \times 1000$$

The LEDset interface is intended to cover a LED driver output current range from 0.05 A to 8 A. The corresponding resistor R_{set} is therefore within the range 100 kOhm to 625 Ohm.

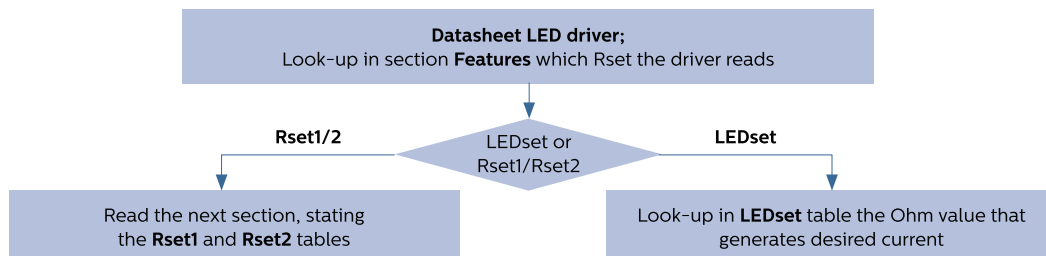In addition, it is possible to add an over temperature protection circuit on the LED module which decreases the setting current in case of an over temperature event and thus limits or folds back the LED driver output current.




Note on E-series: in electronics, international standard IEC 60063 defines preferred number series for amongst others resistors. It subdivides the interval between subsequent values from 1 to 10 into 6, 12, 24, 48, 96 etc. steps. These subdivisions ensure that when some arbitrary value is replaced with the nearest preferred number, the maximum relative error will be on the order of 20%, 10%, 5%, 1% etc.

LEDset – E96 series: table with E96 resistor values

LEDset [Ω]	Idrive [mA]	LEDset [Ω]	Iset [mA]	LEDset [Ω]	Iset [mA]	LEDset [Ω]	Iset [mA]
open	driver's default current	23700	211	11000	455	5110	978
49100	102	23600	212	10700	467	4910	1018
48700	103	23200	216	10500	476	4870	1027
47500	105	22100	226	10200	490	4750	1053
46400	108	21600	231	10000	500	4640	1078
45300	110	21000	238	9760	512	4530	1104
44200	113	20500	244	9530	525	4420	1131
43200	116	20000	250	9310	537	4320	1157
42200	118	19600	255	9090	550	4220	1185
41200	121	19100	262	8870	564	4120	1214
40200	124	18700	267	8660	577	4020	1244
39200	128	18200	275	8450	592	3920	1276
38300	131	17800	281	8250	606	3830	1305
37400	134	17400	287	8060	620	3740	1337
36500	137	16900	296	7870	635	3650	1370
35700	140	16500	303	7680	651	3570	1401
34800	144	16200	309	7500	667	3480	1437
34000	147	15800	316	7320	683	3400	1471
33200	151	15400	325	7150	699	3320	1506
32400	154	15000	333	6980	716	3240	1543
31600	158	14700	340	6810	734	3160	1582
30900	162	14300	350	6650	752	3090	1618
30100	166	14000	357	6490	770	3010	1661
29400	170	13700	365	6340	789	2940	1701
28700	174	13300	376	6190	808	2870	1742
28000	179	13000	385	6040	828	2800	1786
27400	182	12700	394	5900	847	2740	1825
26700	187	12400	403	5760	868	2670	1873
26100	192	12100	413	5620	890	2610	1916
25500	196	11800	424	5490	911	2550	1961
24900	201	11500	435	5360	933	2490	2008
24300	206	11300	442	5230	956	short	driver's max. current

Datasheet LED driver;
Look-up in section **Features** which Rset the driver reads

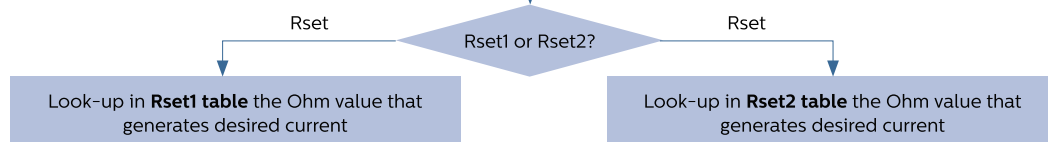If both Rset1 and Rset2 are supported,
Rset2 is advised for future compatibility



Note on E-series: in electronics, international standard IEC 60063 defines preferred number series for amongst others resistors. It subdivides the interval between subsequent values from 1 to 10 into 6, 12, 24, 48, 96 etc. steps. These subdivisions ensure that when some arbitrary value is replaced with the nearest preferred number, the maximum relative error will be on the order of 20%, 10%, 5%, 1% etc.

Note: next page shows extended Rset2 table: E96 values, stating smaller increments

Rset1 – E24 series

Ret1 [Ω]	Iset [mA]	Ret1 [Ω]	Iset [mA]	Ret1 [Ω]	Iset [mA]	Ret1 [Ω]	Iset [mA]
39	200	510	292	6k8	583	91k	690
43	201	560	300	7k5	591	100k	691
47	202	620	309	8k2	599	110k	692
51	203	680	318	9k1	60	120k	693
56	204	750	327	10k	614	130k	693
62	206	820	336	11k	621	150k	695
68	208	910	347	12k	627	160k	695
75	209	1k	358	13k	632	180k	696
82	210	1k1	369	15k	640	200k	696
91	212	1k2	379	16k	643	220k	697
100	215	1k3	388	18k	649	240k	697
110	217	1k5	406	20k	654	270k	698
120	219	1k6	414	22k	658	300k	698
130	221	1k8	429	24k	661	330k	698
150	226	2k	442	27k	665	360k	699
160	228	2k2	455	30k	669	390k	699
180	232	2k4	466	33k	671	430k	699
200	236	2k7	481	36k	674	470k	699
220	240	3k	494	39k	676	510k	699
240	244	3k3	505	43k	678	560k	700
270	250	3k6	517	47k	680	620k	700
300	256	3k9	525	51k	682	680k	700
330	261	4k3	536	56k	683	750k	700
360	267	4k7	546	62k	685	820k	700
390	272	5k1	555	68k	686	910k	700
430	279	5k6	564	75k	688	1M	700
470	286	6k2	574	82k	689	No Rset	default

Rset2 – E24 series

Ret1 [Ω]	Iset [mA]	Ret1 [Ω]	Iset [mA]	Ret1 [Ω]	Iset [mA]	Ret1 [Ω]	Iset [mA]
short	100	430	245	2k	733	9k1	1558
100	100	470	261	2k2	780	10k	1604
110	106	510	277	2k4	823	11k	1653
120	111	560	297	2k7	884	12k	1694
130	116	620	318	3k	941	13k	1730
150	121	680	340	3k3	993	15k	1793
160	130	750	368	3k6	1042	16k	1817
180	13	820	392	3k9	1086	18k	1864
200	146	910	422	4k3	1143	20k	1902
220	155	1k	452	4k7	1192	22k	1935
240	166	1k1	485	5k1	1238	24k	1965
270	176	1k2	515	5k6	1293	27k	2000
300	190	1k3	545	6k2	1350	No Rset	default
330	204	1k5	602	6k8	1402		
360	215	1k6	632	7k5	1454		
390	228	1k8	684	8k2	1503		


Rset priority behavior for drivers that read both Rset1 and Rset2

Rset1	Rset2	Driver status
Open	Open	Driver's default current (see datasheet)
Rset	Open	Rset1
Open	Rset	Rset2
Rset	Rset	Rset2
Short	Open	Rset1 (driver's minimum current, see datasheet)
Short	Short	Rset2 (driver's minimum current, see datasheet)
Open	Short	Rset2 (driver's minimum current, see datasheet)

Please refer to the datasheet of the driver you use to find which Rset or Rsets the driver actually reads.


Rset2 – E96 series: table with E96 resistor values, stating smaller increments but covering same range as the E24 series on previous page

Rset2 [Ω]	Iset [mA]	Rset2 [Ω]	Iset [mA]	Rset2 [Ω]	Iset [mA]	Rset2 [Ω]	Iset [mA]	Rset2 [Ω]	Iset [mA]	Rset2 [Ω]	Iset [mA]
short	min.	255	171	665	335	1740	669	4530	1171	11800	1686
100	100	261	173	681	341	1780	679	4640	1185	12100	1698
102	101	267	175	698	347	1820	689	4750	1198	12400	1708
105	103	274	178	715	354	1870	701	4870	1212	12700	1719
107	104	280	181	732	361	1910	711	4910	1216	13000	1730
110	105	287	184	750	368	1960	724	5110	1239	13300	1739
113	107	294	187	768	374	2000	733	5230	1253	13700	1752
115	108	301	191	787	381	2050	745	5360	1267	14000	1761
118	110	309	194	806	387	2100	757	5490	1281	14300	1771
121	111	316	197	825	394	2160	770	5620	1295	14700	1783
124	113	324	201	845	400	2210	782	5760	1308	15000	1793
127	115	332	204	866	407	2320	806	5900	1322	15400	1802
130	116	340	207	887	414	2360	815	6040	1335	15800	1812
133	118	348	210	909	422	2370	817	6190	1349	16200	1822
137	119	357	214	931	429	2430	829	6340	1362	16500	1829
140	120	365	217	953	436	2490	841	6490	1375	16900	1838
143	122	374	221	976	444	2550	853	6650	1389	17400	1850
147	123	383	225	1000	452	2610	865	6810	1403	17800	1859
150	125	392	229	1020	459	2670	877	6980	1415	18200	1867
154	127	402	233	1050	469	2740	891	7150	1428	18700	1877
158	129	412	237	1070	475	2800	903	7320	1441	19100	1885
162	131	422	241	1100	485	2870	916	7500	1454	19600	1894
165	132	432	246	1130	494	2940	929	7680	1467	20000	1902
169	134	442	250	1150	500	3010	943	7870	1480	20500	1910
174	136	453	254	1180	509	3090	956	8060	1493	21000	1918
178	137	464	259	1210	518	3160	968	8250	1506	21600	1928
182	139	475	263	1240	527	3240	982	8450	1518	22100	1936
187	141	487	268	1270	536	3320	996	8660	1531	23200	1952
191	143	491	270	1300	545	3400	1009	8870	1544	23600	1959
196	145	511	278	1330	554	3480	1022	9090	1557	23700	1960
200	146	523	282	1370	565	3570	1037	9310	1569	24300	1968
205	148	536	287	1400	574	3650	1049	9530	1580	24900	1975
210	151	549	292	1430	582	3740	1062	9760	1592	25500	1982
216	153	562	297	1470	594	3830	1075	10000	1604	26100	1989
221	155	576	302	1500	602	3920	1088	10200	1614	26700	1996
232	161	590	307	1540	614	4020	1103	10500	1629	27000	2000
236	163	604	313	1580	626	4120	1117	10700	1639	open	default
237	164	619	318	1620	638	4220	1131	11000	1653		
243	167	634	323	1650	645	4320	1145	11300	1666		
249	169	649	329	1690	656	4420	1158	11500	1674		

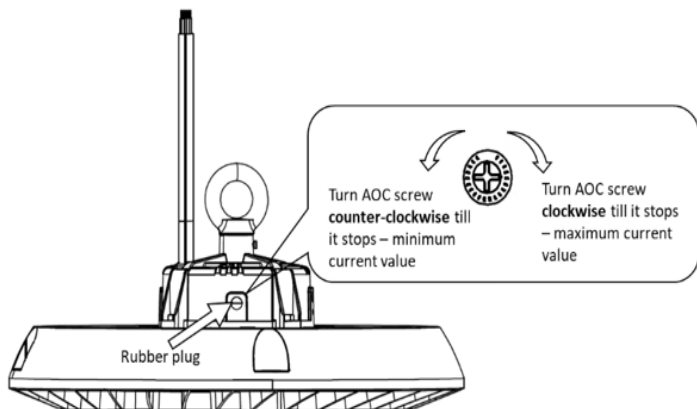

How to... Set the output current via Potentiometer

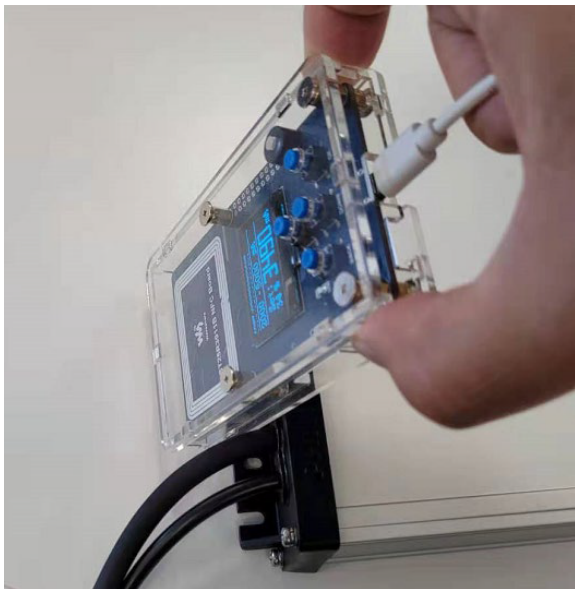Potentiometer in driver provides an easy way to tune the resistor to change the output current. Remove rubber plug in driver to get access to the AOC screw. Use screwdriver to turn it. Then change the output current according to the monitoring value on a multimeter. After setting the current, put the rubber plug back to guarantee the water proof function of the driver.



How to... Set the output current via E-set tool

EP drivers provide an more convenient way to set output current. NFC technology are introduce for this driver family. Use an E-set tool can change AOC quickly without driver power on.

For more information please read "E-set tool get started guided" to get a step by step guidance of how to use it.

How to... Program the output current


The Xitanium Programmable drivers offer a full range of controls, enabling customizable luminaire design and performance. It is possible to control light output levels, preset dimming protocols and set system specifications in the factory and even in the complete installations in the field. This can be done with the Philips MultiOne configurator software. The MultiOne configurator software is an intuitive tool that unlocks the full potential of all programmable drivers from Philips, ensuring that the driver performance matches the needs of the lighting solution. It offers unprecedented flexibility, before, during and after the product installation.

Connecting to a programmable driver

Xitanium Programmable LED drivers are programmed via the Philips MultiOne configurator software. To do so, the driver must be connected to the computer via the MultiOne hardware interface.

For more information and latest version please visit www.philips.com/multione.

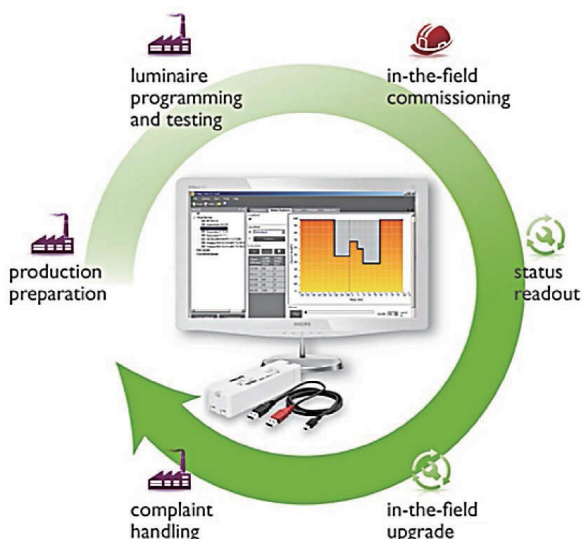This site contains detailed information on how to install the software and how to program the driver.



Mains voltage luctuations

The driver is able to withstand high and low mains voltages for limited periods of time.

Allowable voltage difference between mains input and control input (LED version)

The majority of our LED-drivers do comply with a voltage isolation difference up to 250V between mains and the Touch and Dim control input, as can be caused by a different phase of the power grid in an installation in the field.

Future drivers might have a value higher than 250 V by design.

Use of LineSwitch in three-phase power 230/400V grids

The Xitanium Xtreme drivers allow for supplying power from another phase than the one controlling the LineSwitch interface

Low mains voltage


A continuous low AC voltage (<202 V) can have an adverse effect on the driver's lifetime. The output power will be limited accordingly. A low voltage will not cause the driver to fail over a maximum period of 48 hours at minimum operating AC voltage and maximum ballast ambient temperature.

High mains voltage


A high mains AC voltage will stress the driver and have an adverse effect on its lifetime (maximum of 264-305 V for a period of 48 hours).

Mains guard function

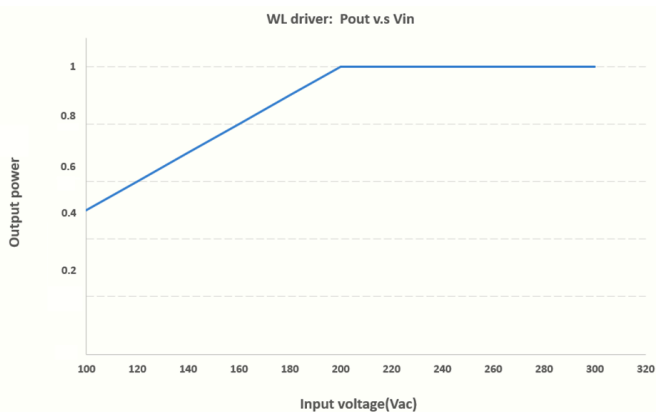The WL series drivers implement mains guard function. Mains guard function can protect driver under low mains voltage by dimming its output power. Please read driver datasheet to learn detail derating curve for each driver. However, a sudden spike in the mains will not be protected by Mains guard.



Derating curve of WL LP 100W driver

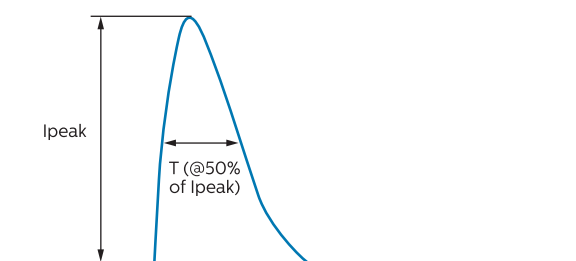

Graphical representation of inrush current

Inrush current

'Inrush current' refers to the briefly occurring high input current which flows into the driver during the initial start-up to charge the capacitors on the input side. Typically, the amplitude is much greater than the operating or steady-state current, as illustrated.

The experimental setup for measuring the inrush current of the Xitanium LED Programmable driver is shown. For the test setup, a line impedance of $645 \text{ m}\Omega / 22 \text{ }\mu\text{H}$ (nom values) is used (NEMA 410 standard requires a line impedance comprised of $450 \text{ m}\Omega / 100 \text{ }\mu\text{H}$ for inrush current measurement). For the measurements, an input DC voltage equal to the peak of the corresponding line voltage is applied (via the capacitor bank).

On a system with an ABB S261 B16 miniature circuit breaker, up to a maximum certain number of Xitanium LED programmable drivers can be connected in parallel without the miniature circuit breaker tripping at driver turn-on. The exact maximum number can be found in the applicable driver datasheet. Please note that the inrush current does not increase proportionally with the number of drivers connected in parallel; i.e. for "N" drivers connected in parallel does not equal "N" times the inrush current for one driver.

MCB type	Rating (A)	Relative number of LED drivers (%)
B	16	100 (stated in datasheet)
B	10	63
B	13.8	1
B	20	125
B	25	156
C	16	170
C	10	104
C	13	135
C	20	208
C	25	260
L, I 1	6	108
L, I 1	0	65
G, U, II 1	6	212
G, U, II 1	0	127
K, III 1	6	254
K, III 1	0	154

Conversion Table for maximum number of drivers on Different types of Miniature Circuit Breakers.

How to... Determine the number of drivers on a MCB

The maximum amount of drivers on a 16A type B Miniature Circuit Breaker (MCB) is stated in the driver's datasheet on www.philips.com/technology.

In the conversion table on the left that stated amount is used as reference (100%).



The maximum quantity of drivers on different types of MCB can be calculated by the reference (see driver's datasheet) × Relative number (last column).

Example;

If datasheet states: max number on type B, 16 A = 20, then for type C, 13 A the value will be $20 \times 135\% = 27$.

Notes

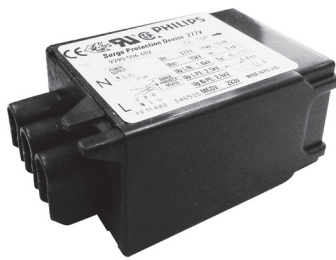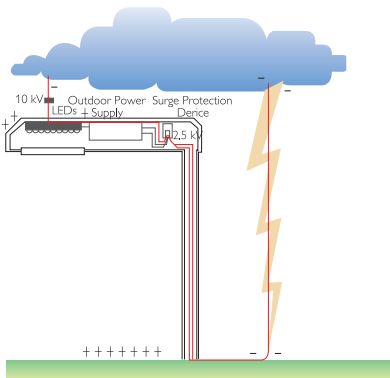1. Data is based on a mains supply with an impedance of 400 mΩ (equal to 15 m of 2.5 mm² cable and another 20 m to the middle of the power distribution) in the worst-case scenario. With an impedance of 800 mΩ the number of drivers can be increased by 10%.
2. Measurements will be verified in real installations; data is therefore subject to change.
3. In some cases the maximum number of drivers is not determined by the MCB but by the maximum electrical load of the installation.
4. Note that the maximum number of drivers is given when these are all switched on at the same time, e.g. by a wall switch.
5. Measurements were carried out on a single-pole MCB. For multiple MCBs it is advisable to reduce the number of drivers by 20%.
6. The maximum number of drivers that can be connected to one 30 mA Residential Current Detector is 30.



Example of SPD

Surge protection

The challenge for Outdoor lighting

Outdoor lighting systems are used in various types of applications, such as street and road lighting, parking areas and tunnels. In many of these installations there is a risk of extreme surges (e.g. lightning strikes). A direct hit will most likely destroy the components in a luminaire. Even an indirect hit near the lighting installation might cause severe damage.

External SPD offers the maximum protection for Outdoor LED investments

Pole-mounted roadway lighting would typically fall into the more severe High Exposure location.

In C62.41.2 standard, for Location Category C (outside, service entrance and equipment), a protection level of 10 kV or more is required. There is almost no way to make the luminaire system surviving without any extra protection.

Installing an external SPD can offer the maximum protection for Outdoor LED luminaire.

Exposure	Standard tests		Optional tests
	1.2/50 μ s Voltage generator Minimum open-circuit voltage to be applied to SPD	8/20 μ s Current generator Current to be driven through the SPD ²	100 kHz Ring Wave for front-of-wave response evaluation
Low	6 kV	3 kA ³	3 kA ³
High	10 kV	10 kA	10 kA

Surge Protection Devices (SPDs) intended for Location Category C

Leakage current

The Xitanium Outdoor LED drivers are designed to meet touch current requirements per IEC 61347-1 standard. The specified maximum values are 0.7 mA peak for IEC and 0.75 mA RMS for UL norms. The test is done with the driver alone. In a luminaire, touch current may be higher, since the LED load may introduce additional touch current.

Precautions may be required on the luminaire level and if multiple drivers are used in a single luminaire.


Electromagnetic compatibility (EMC)

Electromagnetic compatibility (EMC) is the ability of a device or system to operate satisfactorily in its electromagnetic environment without causing unacceptable interference in practical situations. Xitanium Outdoor LED drivers meet EMC requirements per CISPR15 ed 7.2. This test is conducted with a reference setup that includes a driver and an LED load/heat sink combination mounted on a metal plate.


Improvement in EMI Performance

The following practical precautions need to be taken into account in a lighting system to minimize EMI:


- Minimize the differential mode loop area of the lamp wires going from the driver to the light source by keeping the wires close together (bundling). This will minimize the magnetic field and reduce the radiated EMI. Long linear light sources are also part of that loop.
- Minimize the common mode parasitic capacitance of the output wiring + light source to earth by keeping the length of the wires between driver and light source as short as possible. Keep the length of the incoming mains wire inside the luminaire as short as possible.
- Keep mains separated from the output wires (do not bundle).
- Do not route any wiring over and/or along the driver enclosure to avoid any coupling/crosstalk with internal components of the driver.
- Do not route any wiring over and/or along the driver enclosure to avoid any coupling/crosstalk with internal components of the driver.
- Ground the lighting system chassis and other internal metal parts to protective earth (class I luminaires), do not let large metal parts electrically insulated from functional or protective earth. Always connect the protective/functional earth/equipotential connector or wire from the driver and use equipotential bonding wires for all large metal parts like driver mounting plate, reflector, heatsink etc. Keep the protective/ functional earth/equipotential wires as short as possible to maximize their effectiveness and use, as much as possible, large metal areas (chassis, mounting plates, brackets) for earthing purposes instead. Establish a reliable electrical connection by using a toothed washer and screw(s) fastened with adequate torque.

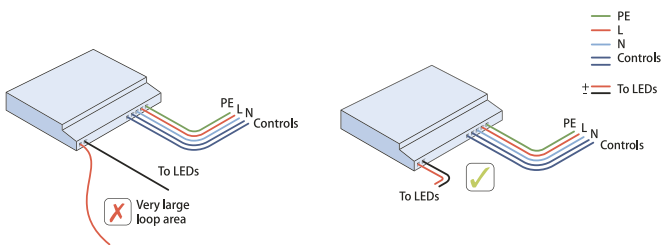


Keeping the wires close together

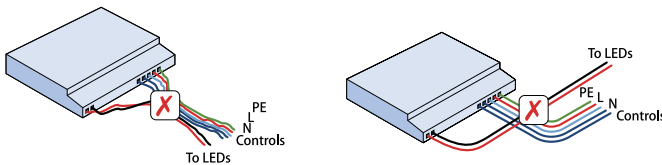

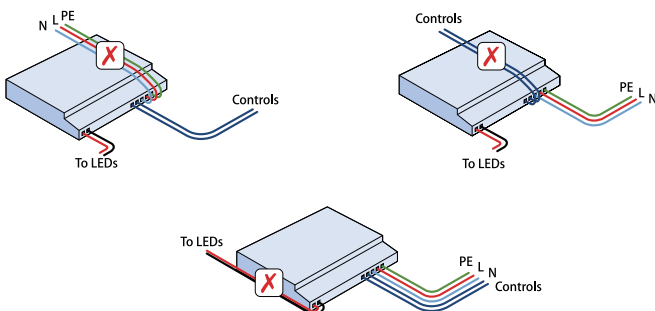Keep mains separated from the output wires



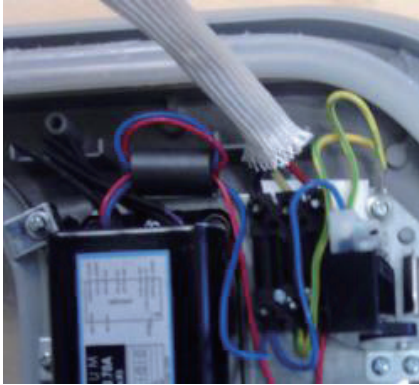Do not route any wiring over and/or along the driver enclosure



Adding ferrite core to wires can improve EMI performance

- For Class II it is advised to establish a functional earth connection between all larger conductive, non-accessible luminaire parts and the driver to remedy potential EMC problems.
- Sometimes, radiated EMC compliance cannot be achieved, necessitating the use of a 100 ... 300 Ω axial ferrite bead(s) for either mains or lamp wiring (effective for interference between 30 MHz and 300 MHz), or coupling the wires through ferrite cores within the luminaire may improve the overall EMC performance. However, selection of the type and characteristics of the additional filter depends on what frequency components have to be damped and by how much.

Adhering to these rules will help in EMC compliance. For further questions, please contact your local Philips representative. Alternatively the Philips Lighting OEM Design-In team could be consulted for a possible solution.


How to... Improve EMI performance

As mentioned before, the total amount of parasitic current needs to be minimized. For that reason, the following practical precautions need to be taken into account in a lighting system to minimize EMI:

- Minimize the Differential Mode loop area of the lamp wires going from the driver to the light source by keeping the wires close together (bundling). This will minimize the magnetic field and reduce the radiated EMI. Long linear light sources are also part of that loop.
- Minimize the Common Mode parasitic capacitance of the output wiring + light source to earth by keeping the length of the wires between driver and light source as short as possible. Also minimize the copper cooling area on the LED PCB and keep the length of the incoming mains wire inside the luminaire as short as possible.
- Keep mains and control wires (DALI, 0-10 V) separated from the output wires (do not bundle).

-
- Ground the lighting system chassis and other internal metal parts to earth (class I luminaires) and do not let large metal parts “float”. Always use the safety or functional earth connector or wire from the lamp driver. Or use equipotential connecting wires for all internal floating metal parts which are inaccessible (class II luminaires). Keep safety and functional earth wires as short as possible to minimize their inductance, use as much as possible large metal areas (chassis, mounting plates, brackets) for earthing purposes instead.
 - For Class II it is advised to establish a functional earth connection between all larger conductive, non-accessible luminaire parts and the driver to remedy potential EMC problems.
 - Sometimes, radiated EMC compliance cannot be achieved, necessitating the use of a 100 ... 300 Ω axial ferrite bead(s) for either mains or lamp wiring (effective for interference between 30 MHz and 300 MHz), or coupling the wires through ferrite cores within the luminaire may improve the overall EMC performance. However, selection of the type and characteristics of the additional filter depends on what frequency components have to be damped and by how much.

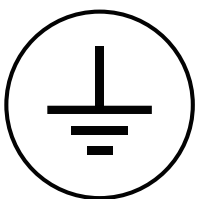Adhering to these rules will help in EMC compliance. For further questions, please contact your local Philips representative. Alternatively the Philips Lighting OEM Design-In team could be consulted for a possible solution.




Symbol for Protective Earth (PE)

Electrical isolation and protective earth

One way to split the Xitanium Outdoor LED drivers is by Class I and Class II driver versions.

Class I drivers

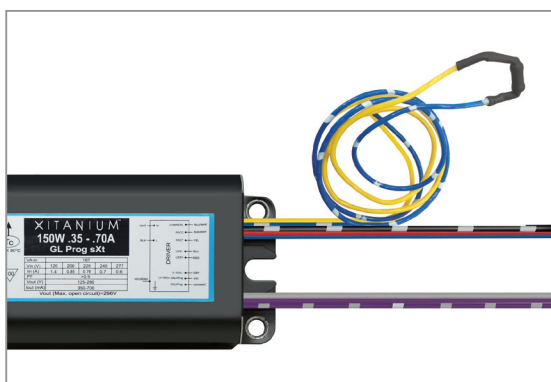These drivers have basic isolation (single isolation foil) between all the electronic circuits and the chassis, hence the presence of the Protective Earth (PE) symbol (see image on the left) on the driver housing.



Example of an insulated Rset

An adequate earth connection must to be made to all electrical conductive parts in the luminaire for Class I driver. The bottom part of the driver housing can be mounted to create earth contact to the luminaire housing, as the earth connector is internally connected to the driver housing. An intermitting earth contact should be prevented, as this is potentially unsafe and can cause a degraded performance. Most drivers in this group typically can generate output drive voltages higher than 60VDC. Always test the quality of your earth contacts between all relevant conductive parts.




Warnings for class I drivers:


- Do not touch any non-insulated live parts, even on the output (secondary) side!
- Any live part on the output (secondary) side should not be touchable during normal operation. This includes the NTC component and Rset component.
- Make sure to insulate the Rset to prevent it from touching the housing.

Class II drivers

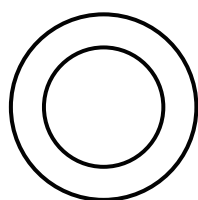Design these drivers are intended for not only built in use, but also for independent use. According to the right symbol, you can find the related one for each application. (Amendment 2 of safety standard IEC61347-1).



Built in version

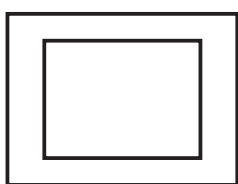

Independent version

Symbol for Double Isolation between input and housing of a driver, in combination with built-in usage.

However, these isolated drivers can be used in both Class I and Class II luminaires under the following conditions:

- When used for Class I, the protective earth connection should be present (see previous section “Class I drivers”).
- When used for Class II, the driver should be incorporated in the luminaire in such a way that
 - a) The driver housing is electrically insulated with respect to electrical conductive materials, such as the housing or reflector and as such not touchable during installation or operation.
 - b) All metal luminaire parts (chassis, heat sink, metallic reflector) connected to the driver housing are not allowed to be accessible by bare hand.
 - c) Any accessible conductive luminaire parts should have basic isolation towards the non-accessible luminaire parts and/or driver housing.


Note: for Class II, EMC requirements should be met without PE connection but need to connect to EQUI joint.

Xitanium LED drivers meet the IEC 61347-1 safety standard

In accordance to this standard, the following safety requirements are met:

- Basic isolation between the Primary and Secondary side wires
- Driver output voltage < 1000VDC
- *Insulation test voltage 1500V (1000V + 2 X 250V)
- Double isolation between all wires and chassis:
Insulation test voltage: 3750V for CCC
3000V for IEC


Thermal Design-In

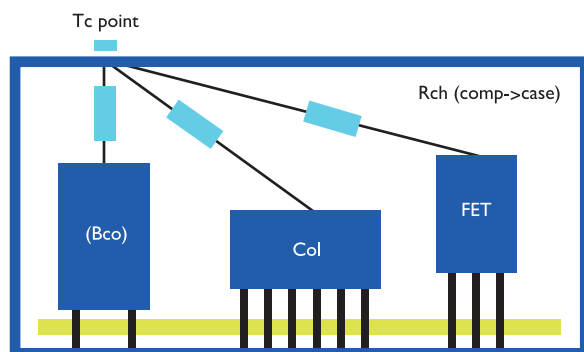

Schematically representation of internal thermal paths to the driver Tc point

Uin: 220-240VAC	Iout: 1.05Adc	150W LED 	LED + BROWN (棕色)
Freq: 50/60Hz	Uout: 62-142Vdc		LED - BLUE (蓝色)
Iin: 0.6-0.83Aac	t _c : 80°C		I-10V + BROWN (棕色)
PF: 0.98	t _a : -40...+55°C		I-10V - BLUE (蓝色) Dimming
Uout (Max. open circuit)= 220Vdc			

Tc point position on driver housing

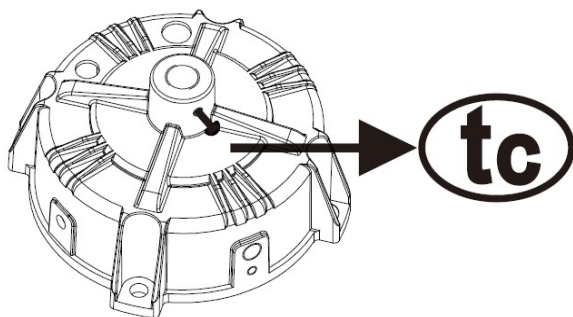

Tc point position on round shape Highbay driver housing

Introduction

This chapter describes the relationship between the Xtanium Outdoor LED drivers in association with Tc point and lifetime.

Definitions

- Case temperature: temperature measured at the Tc point of the driver
- Ambient temperature (Tamb): temperature outside the driver
When switched off >2 hours, temperature at Tc point is likely to equal Tamb

Case Temperature Point (Tc point)

To achieve optimal lifetime and reliability, it is critical that the temperature of the components in the driver remains within its rating. In the LED driver design, all precautions are taken to ensure that the components within the driver are at the lowest possible temperatures.

All temperature measurements are related to a Tcase point (Tc) on the driver. Tc is a reference for the temperatures of the critical internal driver components. The location of the Tc point is identified on the product label. Tc point is marked by the sign on the label of the driver.

Since there is a direct relation between the case temperature (Tc) and the driver components inside the driver, it is sufficient to measure the temperature at the Tc point of the LED driver. This Tc point must not exceed the maximum values stated in the associated datasheet in the download section on www.philips.com/technology

The temperatures as stated above are only valid for a situation where the driver is only cooled via the bottom surface.

How to... Measure Tc at the Tc point

The location of the Tc point is identified on the product label. Tc point is inside the dot or on the side of the case at the location of the pointed arrow (See ellipse in figures on the left). The temperature can be measured using for example a thermocouple that is firmly glued to the driver housing. For a representative measurement the temperature must be stable before any reliable data can be obtained (typically > 0.5 hours).

Relation between Tc and ambient temperature

The Tc increases by approximation linear with the ambient temperature (Tamb). The temperature offset between Tamb and Tc depends on the thermal design of the luminaire. The Xitanium Outdoor LED driver has been designed for outdoor use. For approved ambient temperature range please check the associated driver datasheet on www.philips.com/technology

Driver lifetime

The lifetime of LED drivers depends on the temperature during operation. This means there is a relationship between the Tc point on the LED driver and its lifetime. Xitanium Outdoor LED drivers have a specified minimum lifetime of 50,000 hours with a minimum of 90% survivors at the specified Tc-max (see also respective datasheet).

Module Temperature Protection (MTP)

NTC and thermal design

This feature helps to protect the LEDs when operated in a hot ambient environment. The thermal design of an LED module/PCB should be designed in such a way that the temperature of the LED board (Tc-life) is not exceeded under normal application conditions. The utilization of a Negative Temperature Coefficient (NTC) component serves the purpose to help achieve the lifetime of the LED module or LED PCB if external thermal influences result in the temperature for lifetime (Tlife) being exceeded. When this occurs the light output will be regulated to remain below the critical temperature by the driver dimming down.

Two NTC part numbers which are supported, while the third option enables correct operation in combination with Philips LED modules.

1. 15 k NTC - Vishay 15 kOhm $\pm$ 2% NTC, B25/85=3700, 2381 615 54153
2. 15 k NTC - Murata 15 k, Part number NCP15XW153E03RC (with a Separate 390 ohms resistor in series with the NTC)
3. On selected Philips LED light engines (currently no LED Lines)


Setting MTP behavior (programmable drivers only)

It is possible to set the temperature at which MTP feature is activated, defined by "MTP warn" and the slope, defined by "MTP max". Using the MultiOne Configurator software the settings can be changed.

Setting the thermal de-rating point via NTC

The LED driver will start reducing the light output when the NTC reaches a value of 2966 Ω . The NTC should be selected such that 2966 Ω represents the desired critical temperature inside your LED module/PCB.

Take for example an LED board with a defined Tc-life of 65 °C. Taking the tolerances of the NTC into account results in ± 5 °C. This gives a typical value for the NTC of 71 ± 5 °C. By choosing this setting of 71 °C, we ensure that the driver will not dim the output, due to a too high temperature, before the module reaches 65 °C. The following graph shows a typical R vs. T curve of an NTC resistor. To match 2966 Ω at this temperature, the NTC of 15 k Ω $\pm 2\%$ has been selected.

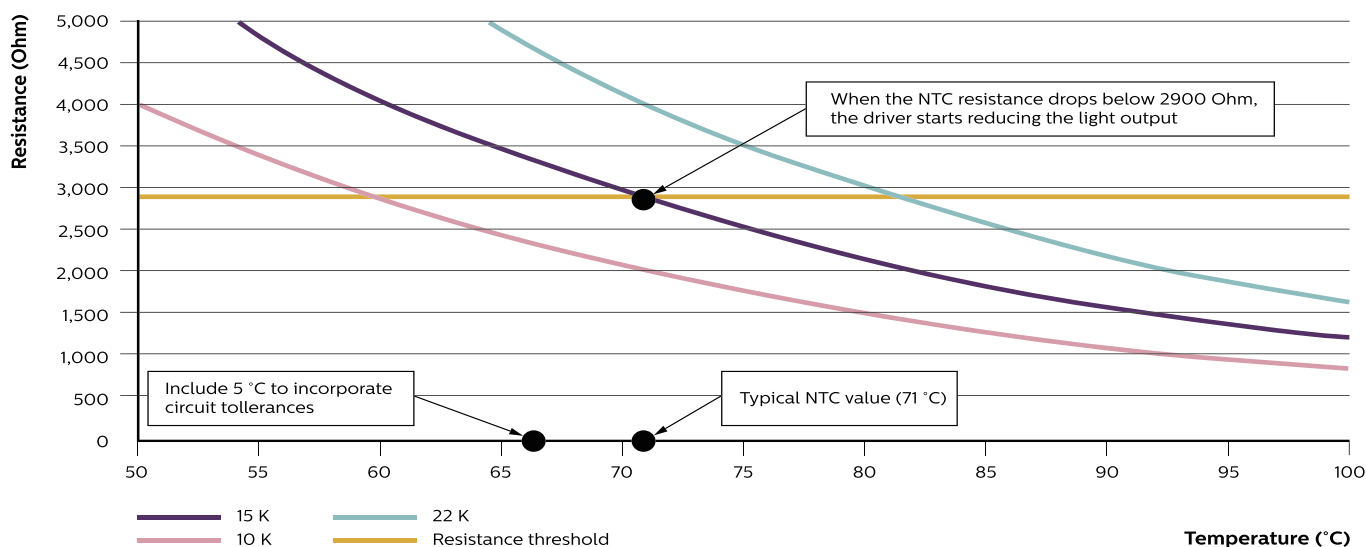

NTC resistance as function of temperature

Mechanical Design-In

IP rating

Below guide should be followed to ensure the right IP rated driver being selected according to OEMs' gearbox type

OEMs' Gearbox	Protection from moisture	IP67	IP66	IP65	Built-in
		IP6X: Dust tight	IP6X: Dust tight	IP6X: Dust tight	N.A
		IPX7: 0.15-1m protected against the effects of immersion	IPX6: protected against the power water jet	IPX5: protected against water jets	N.A
No gearbox	Water immersion longer than 30 mins	✗	✗	✗	✗
	Water immersion less than 30 mins	✓	✗	✗	✗
	Water jets	✓	✓ *	✗	✗
	Water splashing	✓	✓ *	✓ *	✗
Open gearbox (with holes)	Water immersion longer than 30 mins	✗	✗	✗	✗
	Water immersion less than 30 mins	✓	✗	✗	✗
	Water jets	✓	✓	✓	✗
	Water splashing	✓	✓	✓	✗
Sealed gearbox (IP65+)	N.A	✓	✓	✓	✓


* For the applications without gearbox protection, the IP66/65 driver has to be mounted in such a manner that it is not directly exposed to external environmental elements such as hailstones, snow, sand storms, etc.

Driver IP mapping for typical application


Application	Gearbox	Applicable Driver IP rating
Road/Tunnel/Flood	w/o gearbox	IP67/IP66
Road/Tunnel/Flood	w/ open gearbox	IP67/IP66
Road/Tunnel/Flood	w/ sealed gearbox(IP65+)	IP67/IP66/IP65/Built-in



IP67 fixed output connector version

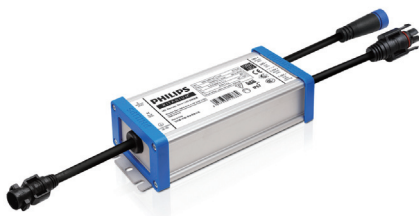

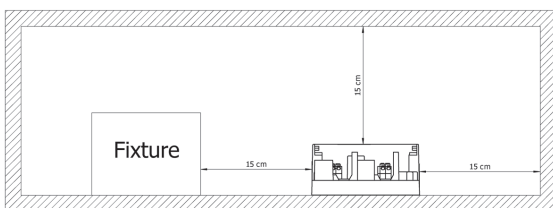IP67 1-10V dimmable output connector version




Installation


To secure the long term reliability of the driver and application, below instructions have to be followed strictly:

For independent drivers

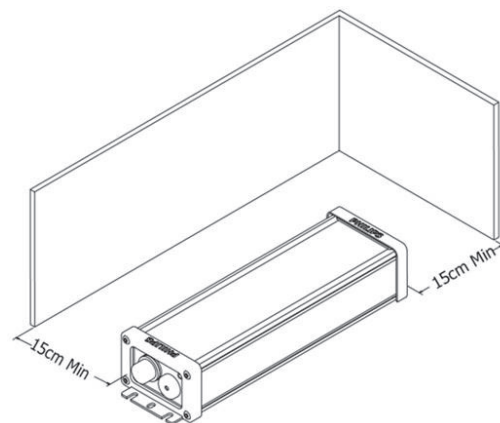
1. It's recommended to mount the driver, including connectors on the cooler area of the luminaire. Verification of the T_c is always mandatory.
2. Putting too much stress on the cables or bending the cables with too much angle can cause seals to leak. The diameter of the bending circle should exceed 25mm.
3. In case driver being used in three-wall condition for the independent application, make sure to keep at least 150mm distance from the body to wall for the sufficient thermal dissipation.



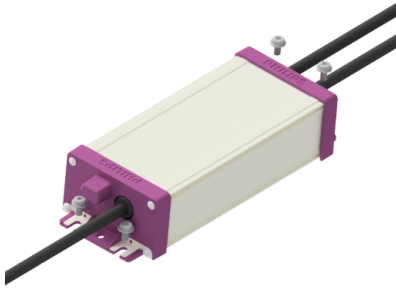4. Make sure to keep the driver dry, acidfree, oilfree, fatfree and at least 15cm distance from the body which is not the mounting surface to wall for the sufficient thermal dissipation and do not exceed the maximum ambient temperature (t_a) stated on the device.
5. The water proof connector has to be fully tightened to prevent the water leaking into the connection in the filed application.
6. Water could be absorbed through the end of cable. The end of cable shall be sealed inside an IP65+ chamber.
7. Intense exposure to sunlight (UV) will make the seals brittle over time causing water leaks. It's recommended to cover the electrical connections to avoid this risk, also to avoid cables being damaged by wildlife.
8. For the additional accessories used in the luminaire, please consider the relevant IP rating.




IP67 independent driver installation

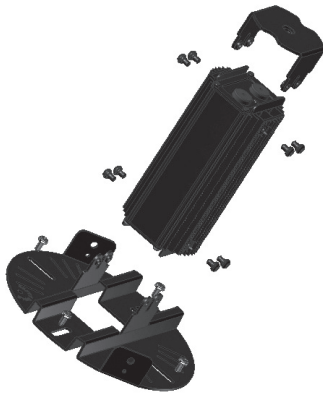

Highbay driver installation



GL RSHB driver and module installation

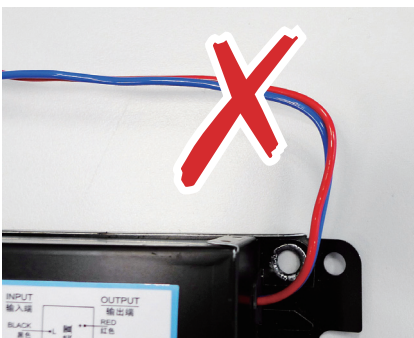

Design-in guide Philips Xitanium Outdoor LED drivers

9. Cannot be used in a marine environment without additional protection against salt.
10. In a Class I system the driver has to be well connected to the protective earth of the installation for safety and reliability consideration.
11. For the independent driver installation, four M4 screws with washer are recommended to be used for driver mounting, recommended torque for screw is 0.9N.m.
12. For the Highbay driver installation, GB818-76 M5x8 Screw is recommended to be used for driver mounting with the top cover and bottom plate.

Notes:

1. Driver is certified to be used with the controls co-located within the Luminaire.
2. In case of the EMI test failure for the independent use, a list of external EMI filter can be offered. Please contact with Philips key account manager or sales representative for support.
3. Driver is only suitable for Class I system.
4. For GL RSHB driver, if UL is required in luminaire, plastic bottom cover can't be exposed. Recommend Signify RSHB module. It can perfectly fit GL RSHB driver. Otherwise adding metal or 5VA flame retardant material to cover it by users.

For built-in drivers

1. The drivers must be installed within a sealed enclosure with IP65+rating.
2. The wires should not be bended more than 3 times in same position, and the bending angle at outlet position should not exceed 60° to prevent wire breaking. A circle is suggested to be used to avoid too much bend angle when we have to make the wires go reverse direction.
3. In actual application, if it's necessary to add extra weight at the wires, eg. bead, the extra weight should be fixed properly so as not to bring extra stress to the wires to avoid the wire break in vibration.
4. The grounding can be achieved via the screw hole. A grooved metal washer is suggested to be used for better grounding reliability.
5. The driver is only suitable for Class I system, so it has to be well connected to the protective earth of the installation for safety and reliability consideration.
6. For the built-in driver installation, four M4 screws with washer are recommended to be used for driver mounting too, recommended torque for screw is 0.9N.m.

Note: Driver is certified to be used with the controls co-located within the Luminaire.



For drivers with connecting lead cables

Where the luminaire is delivered with connecting leads (tails) and without a means of connection to the supply, the manufacturer of the luminaire shall specify which terminal block may be used which shall conform to IEC 60998-2-1 or IEC 60998-2-2; either the terminal block to be used shall be specified or the following shall be defined:

- To comply with the safety regulations, it is recommended to use the IP rated connectors which is same or higher than the driver.
- Rated voltage and current are recommended to follow the spec of the driver.



Controllability

Control characteristics

Control input

Regulating level	100% down to 10%
(module dimming)	100% down to 5%
	100% down to 1% (H2-2013)
	The driver's dimming range is stated in the respective datasheet on www.philips.com/technology .
	The control input complies with EN 60929 (Annex E) and is compatible with Philips Lighting control equipment

Standby power consumption < 500 mW

Control input insulation, basic ≥ 1500 V AC

Dynamic resistance

The Xitanium drivers are designed to driver and dim LED loads with a specified minimum dynamic resistance of the load, stated in the drivers' datasheet. This has been tested and released with the Philips Fortimo LED modules. LED loads which have a dynamic resistance outside the specification of the driver may cause instabilities and should not be used in combination with this driver.

When instabilities during deep dimming (e.g. to 1%) are observed, it is recommended to increase the minimum dim level by adjusting the DALI minimum dim level.

Non-dimmable

The current of the non-dimmable Xitanium drivers can be set with Rset within the operating window. During normal operation, the set current cannot be changed.



LED driver with 1-10V dimming interface




LED driver with 1-10V dimming interface

1-10V Dimming


1-10V is a commonly used dimming interface for LED drivers. The interface requires 2 wires (1-10V + and -) to connect an LED driver to a 1-10V dimmer. The LED driver provides approximately 150 μ A sourcing current to the dimmer. A dimming curve is shown in Figure left.

Note that the output current at 100% level is determined by the driver. The minimum current that can be supplied by the driver is specified in the datasheet. The lowest dim level is defined by the higher of the two values: Minimum output current or 10% dim level for outdoor drivers.

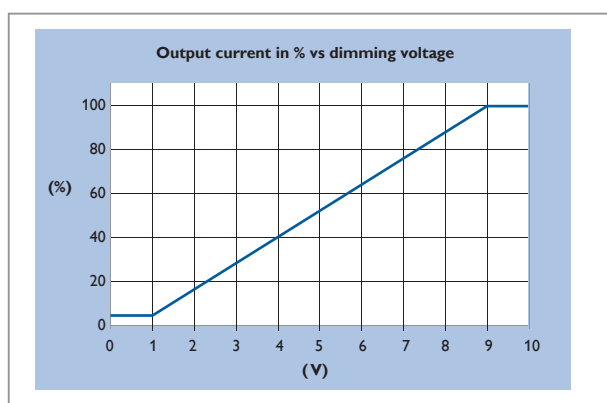
When long dimming wires are required in some applications, maximum length of the dimming wires can be estimated based on voltage drop on the dimming wires. The recommended max voltage drop on the two wires is 100mV.



Output current in % vs dimming voltage

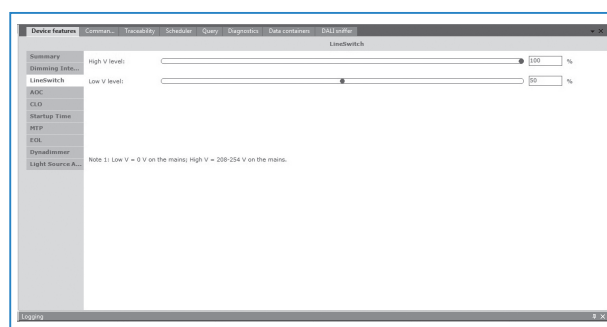

Programming 1-10V dimming

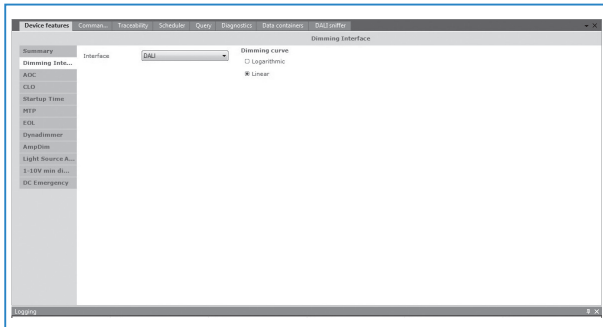

Programming DALI

DALI

Digital Addressable Lighting Interface, or DALI, is a digital communication protocol popular in the lighting industry. It is an IEC standard and there are many control devices from Philips and other manufacturers that communicate using DALI. The voltage across DALI wires is typically 16V (refer IEC specification for details) and it is polarity insensitive. The DALI wires can be run alongside input main wires and the maximum current on a DALI line is limited to 250mA.

Using DALI, it is possible to send dimming commands (1-254 levels), set fade rates and fade times, query driver or LED status, etc. Linear drivers also respond to LED-specific DALI commands e.g. query if the LED module is short circuit or open circuit; select between logarithmic or linear dimming curves, etc. Typically up to 64 DALI drivers can be on one DALI bus.


For more information on DALI, refer to the IEC specification for DALI protocol.

- **IEC 62386:**
102 – General requirements – Control gear
- **IEC 62386:**
207 – Particular requirements for control gear – LED modules.

PWM

The PWM dimming protocol takes a 5V 250Hz (± 25 Hz) PWM as the input signal, and controls the LED current according to the duty cycle. It provides the best balanced to our customers in designing their dimmers and lighting systems, and can be expected to hold some sales volume in the marketplace.

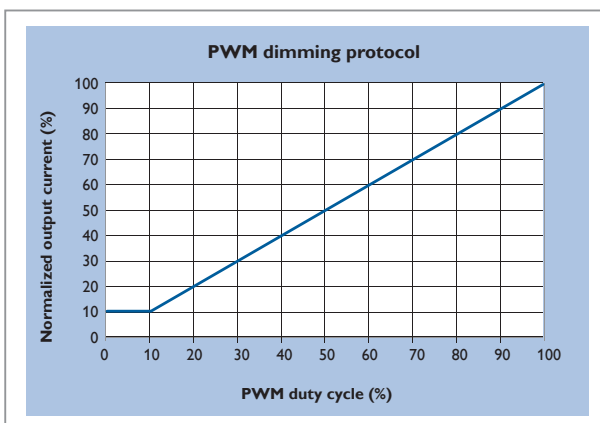- Simplicity (voltage levels compatible with microcontroller; low frequency PWM)
- Flexibility (auxiliary power supply given by LED driver; dimmer can be built up for more complex tasks like networking, GPRS, etc)



This document summarizes the design process of the PWM dimming interface and discusses some critical points in detail, attempts to make a standard building block out of it. However, every design has its special case that some part of the standard circuit may not apply. So the author also tries to point out reasons why such things came into being, as much as he can, aiming to help the readers to figure out solutions in their own work. But still the author cannot cover all aspects even for this very topic, limited by his knowledge and ability.


Integrated programmable dimming protocols

Integrated Dynadimmer


Dynadimmer is an external dimming control device developed by Philips that enables a simple, pre-programmed multistep dimming. Programmable drivers offer an integrated version of this feature.

Integrated Dynadimmer allows dimming to predefined light levels based on the nightly operating time. With flexibility in setting time and light levels, the user can configure the driver for specific locations and application needs. Using Integrated Dynadimmer, it is possible to set up to 5 dim levels and time intervals. The driver does not have a real time clock. Instead it runs a virtual clock, determined by the length of nightly operating hours. After 3 ON-OFF cycles, the driver will calculate the virtual clock time. A valid ON-time is defined as a period during which the driver operates continuously for ≥ 4 hours to ≤ 24 hours. As shown in Figure 24, after repeating the driver ON-time for 3 consecutive days, the dim profile takes effect from the 4th day onwards. For more information on Dynadimmer scenarios please refer to Chapter 15.

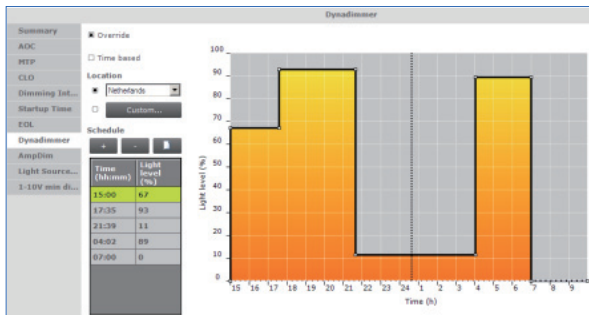
Newer driver types allow setting the predefined light level as low as 0% (OFF); in the near future all drivers will offer this option.




Integrated Dynadimmer settings

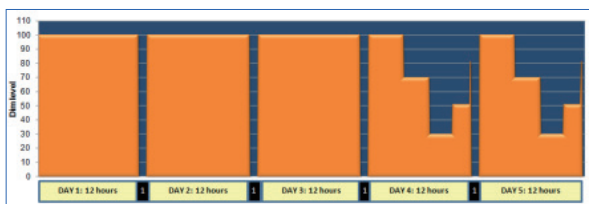

Dynadimmer virtual clock setting

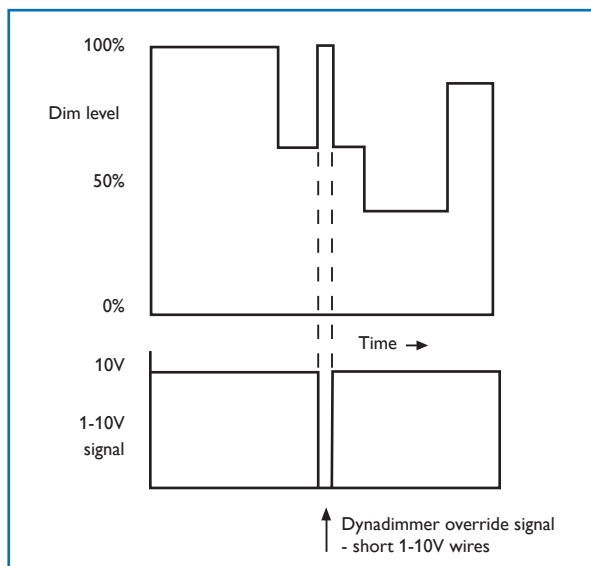


Dynadimmer override signal

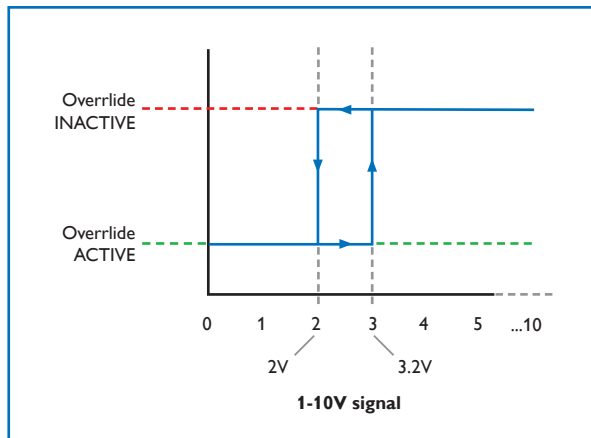

Dynadimmer voltage threshold

Dynadimmer Override

In some instances, there is a need to override the Dynadimmer dim cycle either manually or automatically. For example, luminaires in a parking garage may be configured to utilize the integrated Dynadimmer feature with a defined dim cycle. A motion sensor can be associated with one or more luminaires which, when activated by passing cars, can signal the driver to override the dim cycle and go to full light output. When the Dynadimmer Override function is enabled and the 1-10 V wires are shorted, the driver will override the active dim cycle and go to full light output. The driver will return to normal Dynadimmer dim cycle when the 1-10 V wires are open. As shown in Figure 25, the 1-10 V wires function as a switch in the Dynadimmer override mode. Figure 26 depicts the voltage threshold necessary to activate the override functionality and the hysteresis margin.

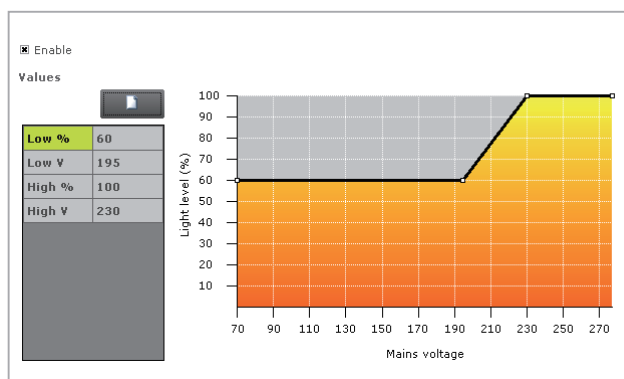

Programming AmpDim functionality

AmpDim

Historically mains dimming was used on magnetic ballasts to dim conventional lamps. By lowering the mains voltage, a proportionate reduction in light output was achieved. Until now electronic ballasts were not able to replicate this function. AmpDim enables cabinet based dimming without the need for additional control wires or infrastructure changes.

A cabinet controller signals to the driver to lower the light output via a reduction in the amplitude of the mains voltage. The intelligence embedded in the LED driver allows for a pre-programming of multiple dimming levels based on the amplitude of the mains voltage.


The default range of AmpDim is 170V – 250V. The range can be customized via the programming interface. It is possible to set the Start Voltage, Start Percent, Stop Voltage, and Stop Percent. Shows an example of the AmpDim programming interface.

Programming note

- There needs to be a minimum of 20V difference between Start and Stop Voltage settings when programming the driver.
- There must be a minimum delta of 5 V in the mains voltage before the driver starts dimming. This prevents accidental dimming due to small fluctuations in the mains voltage.

Parameter	Min	Max	Increments
Start Voltage	170 V	250 V	1 V
Stop Voltage	150 V	230 V	1 V
Start Percent	30%	100%	1%
Stop Percent	30%	100%	1%
Start Voltage - Stop Voltage	20 V	100 V	

AmpDim programming parameters

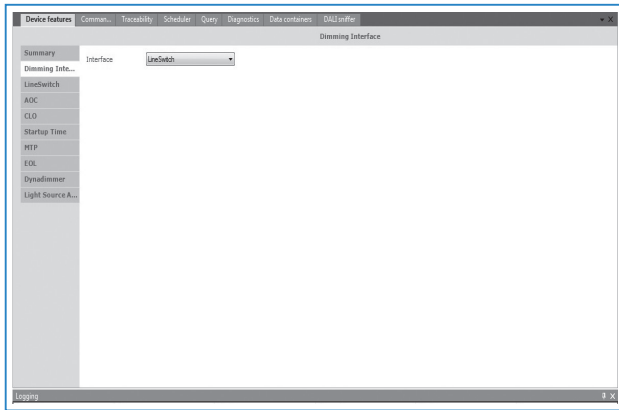

LineSwitch

The LineSwitch feature operates by using the extra mains pilot line. This is a one-step dimming solution which enables dimming of groups of light points to a predefined level with only a simple switch controlled by a timer, presence detector etc.

Dimming to the desired level can be achieved by applying mains voltage to the LineSwitch driver input.

The pilot line wiring must be rated for the applied mains voltage. Copper diameter is not critical because this is a signal line with negligible current draw.

The driver mains input wiring is line- and neutral-polarized and its polarity should be observed.

The total pilot line cable length should not exceed 56m per driver based on a common parasitic cable capacitance of 100 pF/m.

The change-over from full light level output to a predefined dimming level can be achieved by either disconnecting the pilot line mains from or applying mains voltage in the range of 220 ... 240V on the pilot line.

This feature can be enabled via the MultiOne Programming software in combination with the USB DALI programmer.

Configurable parameters are:

- Light Output in % when mains voltage (High V level) is present at the LineSwitch input:
- Light Output in % when no mains voltage is present (Low V level) at the LineSwitch input



Philips MultiOne hardware interface

How to... Connect to and program driver

Connecting to a programmable driver

Xitanium Outdoor drivers are programmed via the Philips MultiOne configurator software. To do so, the driver must be connected to the computer via the MultiOne hardware interface.

This can be done with Programmable drivers only.
Check the datasheet for the driver's ability on www.philips.com/technology.

For the latest version of the MultiOne configurator software please check www.philips.com/multione.

How to... See the programming taking effect

Programming time

Depending on the selected features to program, the programming time varies between 2 up to about 15 seconds. It is possible to program up to 64 drivers at the same time. In case of group programming there is no individual confirmation (verification) from each driver.

In order to have the programmed values take effect for Xitanium programmable LED drivers, the mains power needs to be cycled. For newer drivers (1% minimum dim level) On/Off via standby is also sufficient.



Example of a shorted DALI interface

Configurability

Introduction

This chapter describes the way you can configure the drivers with the MultiOne Configurator:

Please check the datasheet of the driver on www.philips.com/technology to know if your driver supports configurability.

The characteristics of the MultiOne configurator are:

- One tool for all Philips configurable drivers: Xitanium LED Indoor and Outdoor drivers; HF-R Indoor fluorescent gear; DynaVision Xtreme HID electronic gear...
- Future proof by design: modular approach, very scalable and backwards compatible
- Provides access to all features built in the driver
- Tool combines configuration with debugging
- Settings of the drivers can be changed any point in the product lifecycle.

This configurator consists of:

1. Philips MultiOne Interface tool
2. USB cable (connection to PC or laptop)
3. Philips MultiOne Software

Philips MultiOne Interface tool

There are 2 versions of MultiOne interface tooling depending on the type of communication:

1. LCN8600/00 MultiOne Interface USB2DALI

The interface that can be used with the MultiOne PC software to commission, configure, diagnose drivers via the DALI interface

2. LCN9600 MultiOne SimpleSet® interface

The interface that can be used with the MultiOne PC software to configure drivers wirelessly using SimpleSet® technology.

Note: The programming of the drivers with SimpleSet must be done while disconnected from mains.

When ordering the MultiOne Interface, the correct USB cable will be supplied with the interface tool. The tool can be ordered via your Philips sales representative or via the Philips OEM webshop, <http://oemwebshop.philips.com>.



MultiOne Interface USB2DALI



MultiOne SimpleSet® interface



Philips MultiOne Software

There are 2 versions of MultiOne Software depending on functionality and location:

1. MultiOne Engineering


Especially developed to access all functionality of the driver; to configure, diagnose and prepare the configuration file for the production environment. Includes also:

- DALI commands, scheduler.
- SimpleSet®.

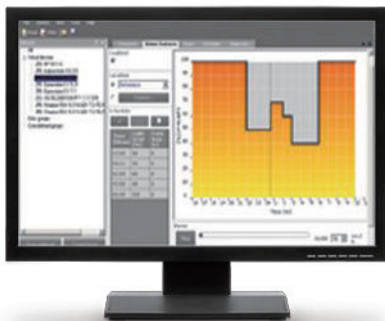2. MultiOne Workflow

Developed to configure all devices or subassemblies in the production environment or field in a simple and quick way.

Get your software (free downloadable) or check if you have the latest version via the website,
<http://www.philips.com/multione>.



System requirements

The MultiOne configurator must be connected to a system with minimum system requirements:

- Windows PC or Laptop
- Microsoft Windows XP + SP3 or Windows 7, Windows 8.0, Windows 8.1
- USB 2.0 ports (preferable two free ports)
- Min 35 MB of free disk space
- Microsoft.NET Framework 3.5 SP1 (!)

Getting Started

Connect the USB cable of the MultiOne Configurator between the PC and the configuration tool.

To install the software, launch the installation file for the latest version and follow the instructions on your screen. The installation wizard will guide through the process of installing the software and will ask where the software needs to be installed, if a shortcut is needed on the desktop and a new program is also created in the Start Menu.

More information on how to program a driver, can be found in getting started and the instruction manual on the website,
<http://www.philips.com/multione>.

MultiOne System



Settings

The Xitanium configurable LED drivers have a fixed set of features and factory settings when supplied. The set of features is defined in the datasheet of the driver.

The default settings of the driver can be found in the driver datasheet in the download section on www.philips.com/technology

Quality and Reliability

Switching & cycling lifetime of LED drivers

Impact of on and off switching on lifetime of electronic drivers in LED systems

In this section a description is presented of the impact of mains voltage switching on the lifetime of electronic drivers in lighting systems. Because switching on and off the lighting has an impact on different failure modes, a distinction has to be made between switching on and off, and thermal cycling.

Electrical failures due to switching Vmains on and off

Before the lighting is switched on in the electronic circuit all capacitors are uncharged. By a simple toggle of the mains voltage all capacitors will be charged, causing peak currents in the circuit. Inductors react to this by creating peak voltages. Occurrence of peak currents & voltages during starting is inevitable. The circuit design and component selection should be of sufficient quality that no components are overstressed during the starting conditions. If the quality is not sufficient, failures will occur at a certain rate over time. The failure rate will be influenced by usage conditions such as temperature and mains voltage. The failure rate will be further enhanced by irregular mains voltage events such as dips, surges or black outs. For a good quality design all conditions and components are carefully checked. In general LED systems and products are designed to withstand >100,000 switches under the specified use conditions.

Mechanical failures due to thermal cycling


A completely different failure mode which is also due to switching on and off the light is the failure of solder joints, due to thermal cycling. Stresses in solder joints are caused by the differences of the thermal expansion coefficients (CTE's) of printed circuit board, solder and component materials.

Due to heating up and cooling down mechanical stresses build up in the solder, which eventually result in cracking and finally failure of the joint. In most cases failure of one solder joint means the end of the product. The solder joint failure mechanism is also referred to as solder joint fatigue. This is a typical wear out failure mechanism with a negligible failure rate for many years, but for which after the typical lifetime has passed, failures come at an accelerated speed.

Electronic Drivers for LED lighting are typically designed to last 50,000 operational hours. The reference for this lifetime is a typical user profile of 10-12 hrs usage and 1 switching on and off every day. For the electrical stresses during switching there is no problem switching many more times, even up to >100,000 times. However for the solder joints there can be a risk for the lifetime of the product.

Impact of thermal cycles per day on the driver lifetime

As the drivers are typically designed to withstand 1 full thermal cycles every day, lifetime will reduce with an increasing cycling frequency. However this reduction will be limited by the heating time of the product in the application. As the heating time of a driver in real applications varies typically between 60 and 120 minutes, maximum and minimum driver temperature will not be reached when the cycling frequency is faster than 60 minutes. Because the solder-joint damage relates to a higher power of the temperature difference between hot and cold condition, the negative effect on lifetime reduces for the higher cycling frequencies. This is expressed in the above graph.

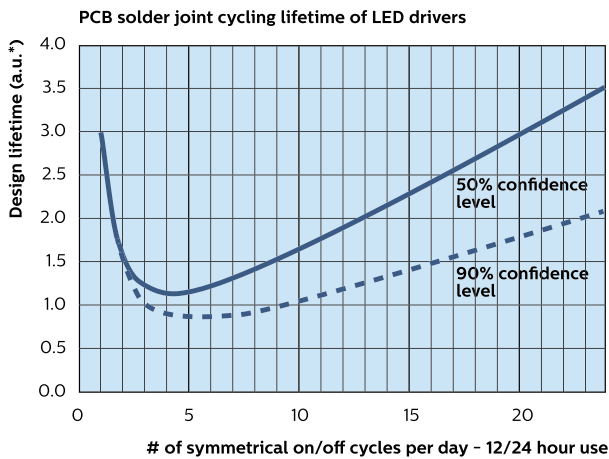

*) arbitrary unit value 1.0 means product design - lifetime will be reached (typical 50,000 h). Longer lifetimes can be limited by other failure modes.

Because of the large variation and differentiation between drivers and applications, it is an impossible task to specify the above graph for every driver and application specifically. Therefore only the critical conditions are listed for which there could be a risk to the cycling lifetime of the driver:

Critical conditions for the driver lifetime due to thermal cycling are:

- Small driver / system (short heating time) without appropriate heat sinking (high T_{max}).
- Large difference between T_{max} and temperature in off state T_{min} (e.g. $> 50\text{ }^{\circ}\text{C}$). See also next paragraph.
- Application @ temperatures $< -40\text{ }^{\circ}\text{C}$ T_{ambient} .

Especially if the above parameters occur in combination with each other there can be a risk for thermal cycling lifetime. To improve cycling lifetime when required, it is most relevant to decrease the T_{max} by appropriate heat sinking of the driver. As a rule of thumb $10\text{ }^{\circ}\text{C}$ diminished ΔT between $T_{\text{case on/off}}$, will add 30% to cycling performance.

Impact of product ambient temperature on cycling performance

In the first approximation the solder joint lifetime is independent of the ambient temperature. The driving parameter for the solder joint failure fatigue is the temperature difference between T_{max} during the 'on' state and T_{min} during the 'off' state. The way the driver is built in to a luminaire is very important as this can decrease the temperature difference. Appropriate heat sinking of the driver is the most effective way to improve the driver cycling lifetime. As a rule of thumb $10\text{ }^{\circ}\text{C}$ diminished ΔT between $T_{\text{case on/off}}$, will add 30% to cycling performance.

Compliance and approval

Driver compliances and approvals can be found in the published driver Declarations of Conformity (DoC) and ENEC/CB certificates as published on www.philips.com/oem. For further questions please contact your local Philips sales representative.

System Disposal

We recommend that the Xitanium LED Outdoor drivers and its components are disposed of in an appropriate way at the end of their (economic) lifetime. The drivers are in effect normal pieces of electronic equipment containing components that are currently not considered to be harmful to the environment. We therefore recommend that these parts are disposed of as normal electronic waste, in accordance with local regulations.

Disclaimer

Philips will perform the testing of the LED systems to high standards of workmanship. The tests are carried out with reference to the EN/IEC standards, if any, which are regarded by Philips as being of major importance for the application of the lamp gear and the lamp within the fixture for horticultural applications.

The design-in guide, regarding the testing and design in of the LED system provided by Philips, is not an official testing certificate, and cannot be regarded as a document for official release of the fixture. The OEM is liable for the official testing by a certified test body and all markings, such as CE and ENEC marks, on the fixture assembly.

The design-in guide is for information purposes only and may contain recommendations for detecting weak points in the design of the system (lamp – lamp gear – fixture), if any.

Specifically mentioned materials and/or tools from third parties are only indicative: other equivalent equipment may be used but it is recommended that you contact Philips for verification.

Philips will not be liable for unforeseen interactions of the proposed solutions when applied in the fixtures or applications using these fixtures. Philips has not investigated whether the recommendations are or will in the future be in conflict with existing patents or any other intellectual property right. Philips does not warrant that its recommendations are technically or commercially the best options.

Since the tests are only performed on one particular fixture provided by the customer, it will be treated as a prototype. This means that there is no statistical evidence regarding later production quality and performance of the lamp – lamp gear – fixture system.

As Philips does not have control over manufacturing of the fixtures, Philips cannot be held liable for the fixture assembly.

Philips will not accept claims for any damage caused by implementing the recommendations.

No warranty whatsoever may be claimed by the OEM with regard to the content and/or quality of the design-in guide or any other advice, or the conclusions and/or recommendations in the design-in guide or any other document, either express or implied, and Philips expressly disclaims any implied warranties of any kind, including without limitation any warranties of satisfactory quality, fitness for a particular purpose or non-infringement and any warranties regarding the design-in guide or any other advice or the use of the results of any activity performed while testing the fixture with respect to its correctness, quality, accuracy, completeness, reliability, performance or otherwise.

The OEM expressly agrees that test design-in guides are provided by Philips on an 'as is' basis and an 'as available' basis at customer's sole risk and expense. Philips shall not be liable for any lost profits or lost savings, indirect, incidental, punitive, special, or consequential damages whether or not such damages are based on tort, warranty, contract, or any other legal theory – even if Philips has been advised, or is aware, of the possibility of such damages.

The OEM must bring any claim for damages within ninety (90) days of the day of the event giving rise to any such claim, and all lawsuits relative to any such claim.



© 2018 Signify Holding, IBRS 10461, 5600VB, NL. All rights reserved.

www.philips.com/Technology

The information provided herein is subject to change, without notice. Signify does not give any representation or warranty as to the accuracy or completeness of the information included herein and shall not be liable for any action in reliance thereon. The information presented in this document is not intended as any commercial offer and does not form part of any quotation or contract, unless otherwise agreed by Signify. Philips and the Philips Shield Emblem are registered trademarks of Koninklijke Philips N.V. All other trademarks are owned by Signify Holding or their respective owners.

30 December, 2021
Data subject to change

Design-in guide - Philips Xitanium Outdoor LED drivers